
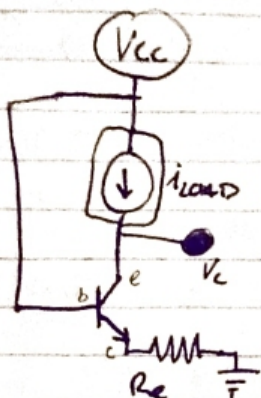

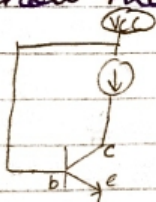
## 1.1 CURRENT SOURCE

In this problem, you will design and analyze a current source to drive a laser diode array from a 12V source.



a) Consider the above circuit. Using the general properties of transistors, show that  $i_{LOAD} = \frac{\beta}{1+\beta} \frac{V_{CC} - 0.6V}{R_e}$



$$V_e = V_b - 0.6V, \quad V_b = V_{CC} \Rightarrow V_e = V_{CC} - 0.6V$$

$$i_e = \frac{V_e}{R_e} = \frac{V_{CC} - 0.6V}{R_e}$$

$$i_e = i_b + i_c = \frac{1}{\beta} i_c + i_c = i_c \left( \frac{1+\beta}{\beta} \right)$$

$$i_c = \frac{\beta}{1+\beta} i_e = i_{LOAD}$$


$$\therefore i_{LOAD} = \frac{\beta}{1+\beta} \frac{V_{CC} - 0.6V}{R_e}$$

b) What emitter resistor  $R_e$  should be used so that the current source provides 2mA? (Assume  $\beta = 100$ , but don't do this in real life -  $\beta$  varies from chip to chip)

$$i_{LOAD} = 0.002A = \frac{100}{101} \frac{(12 - 0.6)V}{R_e} \quad (\Rightarrow R_e = \frac{100}{101} (11.4V) \left( \frac{1}{0.002A} \right) = 5643.564\Omega$$

$$\Rightarrow R_e \approx 5.64 k\Omega$$

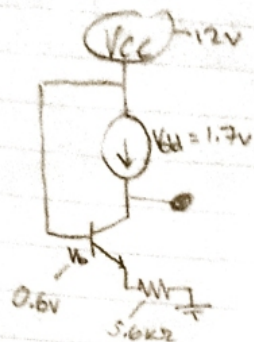1.c) Using this value for  $R_e$ , a red diode is placed as the load, w/  $V_{diode} = 1.7V$ . What is the voltage at the collector and the current through the diode?



$$V_c = 12 - 1.7 - 0.6 = 9.7V$$

$$\Rightarrow i_{load} = \frac{100}{101} \frac{V_e}{R_e}$$

,  $V_e = 9.7$  (as the base voltage has been accounted for)  
 $R_e = 5.6k\Omega$

$$i_{load} = \frac{100}{101} \frac{9.7}{5643\Omega} = 0.001701754A$$

$$\boxed{i_{load} \approx 1.7mA}$$

$$\boxed{V_c = 9.7V}$$

d) Now a string of LEDs is used. How many LEDs can be used (in series) so that they all remain lit up? What is the voltage at the base as a function of # of LEDs, up to the point where they all turn off?

$$\frac{(12 - 0.6)V}{1.7V} = 6.70588 \Rightarrow 6 \text{ LEDs can be connected in series.}$$

If any more, there will not be enough voltage to overcome the  $V_b$  needed to power the transistor.

$$V_b(n) = 11.4V - 1.7n, \quad n = \# \text{ LEDs}, \quad n \leq 6$$

e) Now place a  $10k\Omega$  potentiometer as the load. Plot the current through the potentiometer and the base voltage as a function of resistance.



## 3 Transistor Based Switch

You are driving a 12 V, 60W heater using an Arduino microcontroller. The Arduino is great for automation and computational logic, but not so great at a power source. The solution, of course, is a transistor. A power transistor is used so that a "beefy" power supply can source the required current at the operating voltage and the Arduino is placed at the base.

- a) First let's choose components. We need a transistor that can safely pass the required components. If the heater is operating at full capacity, (12V, 60W), what is the required current?

$$P = iV, \quad i = \frac{60W}{12V} = \boxed{5A = i_c}$$

- b) Let's pick a power transistor. Find a npn transistor that can handle this current and voltage. Look at the datasheet for the following models: PN2222A, 2N31A, MJF15030G. Is there sufficient max collector current in any of these models? If so, which one? If not, try to find a better model.

MJF15030G has max collector current  $i_c = 8A$ ,  $V_{CE} = 5V$

- c) Assuming  $\beta = 100$ , what value of base resistor,  $R_b$ , should be chosen such that the transistor is saturated at 50% of the current from part a)?


Want saturated (aka turned on) at  $0.25A = i_c$

Turned on when  $V_c > V_b$

$$i_b = \frac{i_c}{\beta} = \frac{2.5A}{100} = 0.025A$$

$$R_b = \frac{V}{i_b} = \frac{15 - 0.6V}{0.025A} = 176\Omega$$

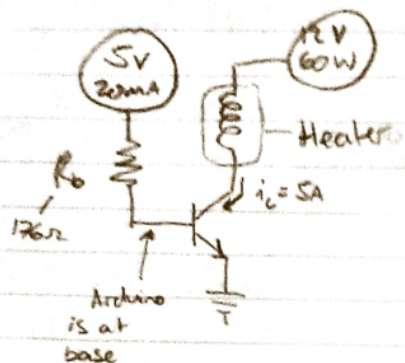d) Setting  $R_0$  to this value, what is the current required of the Arduino when  $i_c$  is as determined in part a)?



$$i_c = 5A$$

$$R_0 = 176\Omega$$

Arduino is placed at the base, so current through arduino is the same as  $i_b$ .

$$\Rightarrow i_{\text{ARDUINO}} = 0.025A$$

e) Create a LTspice simulation and verify results.

f) This is still a bit much so we'll do a trick to make it easier on our poor little arduino. This is similar to a "Darlington Pair" diagrammed in the insert of Figure 7b). In this case you can get away w/ a much larger base resistor and therefore smaller base current while remaining in saturation. Simulate this circuit in spice and find out how large  $R_0$  can be before the current drops below  $i$  from part a). What current is the Arduino supplying in this case?

$$i_c \geq 5A$$

$$\text{Max } R_0 = 6300\Omega \text{ (see Figure 2)}$$

$$i_b = i_{\text{ARDUINO}} = 0.50 \text{ mA}$$

